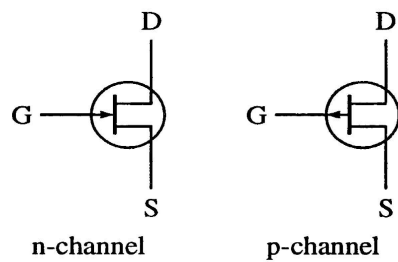


Solution Tutorial 2

BJTs, Transistor Bias Circuits, BJT Amplifiers, FETs and FETs Amplifiers

Part 2: FETs and FETs Amplifiers

1. Sketch the schematic diagrams for a p-channel and an n-channel JFET. Label the terminals.



2. A certain p-channel JFET has a $V_{GS(off)} = 6\text{ V}$. What is I_D when $V_{GS} = 8\text{ V}$?

Since $V_{GS} > V_{GS(off)}$, the JFET is off and $I_D = 0\text{ A}$.

3. Using the curve in Figure 1, determine the value of R_S required for a 9.5 mA drain current.

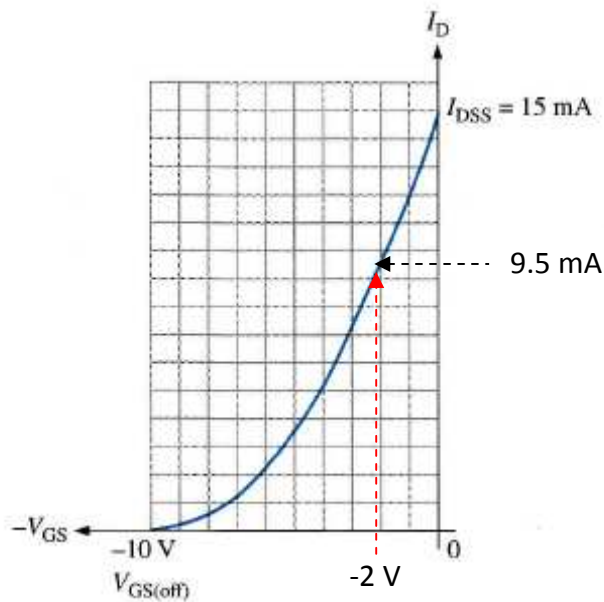


Figure 1

From the graph, $V_{GS} \cong -2\text{ V}$ at $I_D = 9.5\text{ mA}$.

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \left| \frac{-2\text{ V}}{9.5\text{ mA}} \right| = 211\ \Omega$$

4. Graphically determine the Q-point for the circuit in Figure 2(a) using the transfer characteristic curve in Figure 2(b).


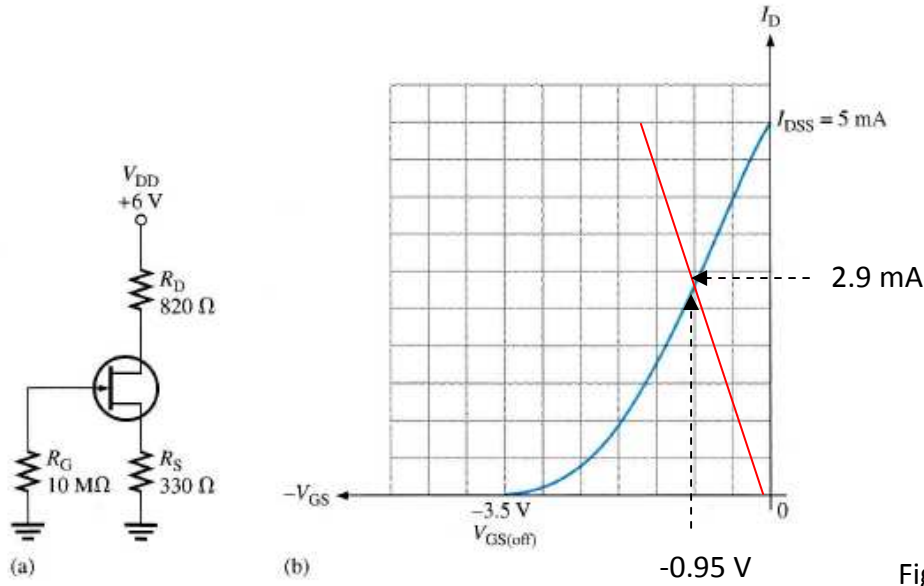


Figure 2

For $I_D = 0$
 $V_{GS} = -I_D R_S = (0)(330 \Omega) = 0 \text{ V}$
 For $I_D = I_{DSS} = 5 \text{ mA}$
 $V_{GS} = -I_D R_S = -(5 \text{ mA})(330 \Omega) = -1.65 \text{ V}$
 From the graph, the Q-point is
 $V_{GS} \cong -0.95 \text{ V}$ and $I_D \cong 2.9 \text{ mA}$

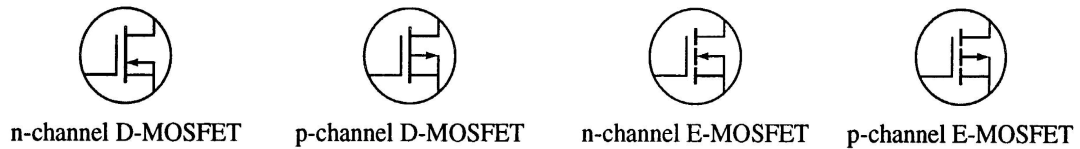5. Sketch the schematic symbols for p-channel and an n-channel D-MOSFETs and E-MOSFETs. Label the terminals.



6. In what mode is an n-channel D-MOSFET with a positive V_{GS} operating?
 An n-channel D-MOSFET with a positive V_{GS} is operating in the **enhancement mode**.
7. Determine I_{DSS} , given $I_D = 3 \text{ mA}$, $V_{GS} = -2 \text{ V}$ and $V_{GS(off)} = -10 \text{ V}$.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$I_{DSS} = \frac{I_D}{\left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2} = \frac{3 \text{ mA}}{\left(1 - \frac{-2 \text{ V}}{-10 \text{ V}} \right)^2} = 4.69 \text{ mA}$$

8. Each E-MOSFET in Figure 3 has a $V_{GS(off)}$ of +5 V or -5 V, depending on whether it is an n-channel or a p-channel device. Determine whether each MOSFET is on or off.

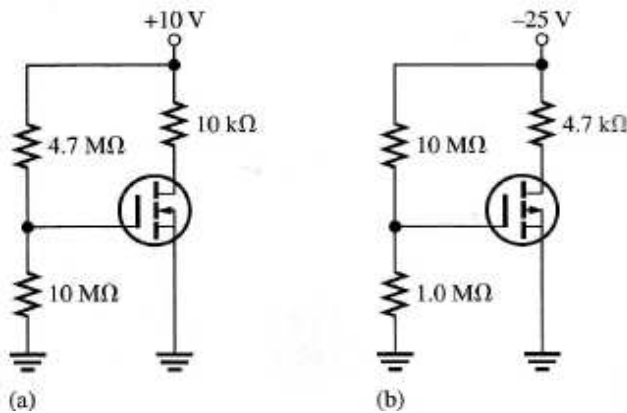


Figure 3

(a) $V_{GS} = \left(\frac{10\text{ M}\Omega}{14.7\text{ M}\Omega} \right) 10\text{ V} = 6.8\text{ V}$ This MOSFET is **on**.

(b) $V_{GS} = \left(\frac{1.0\text{ M}\Omega}{11\text{ M}\Omega} \right) (-25\text{ V}) = -2.27\text{ V}$ This MOSFET is **off**.

9. The gain of certain JFET amplifier with a source resistance of zero is 15. Given $g_m = 2300\ \mu\text{S}$, calculate the drain resistance.

$$A_v = g_m R_d$$

$$R_d = A_v / g_m = 15 / 2300\ \mu\text{S} = 15 / (2300 \times 10^{-6}\ \text{S}) = 6.52\ \text{k}\Omega$$

10. Determine the voltage gain of each common-source amplifier in Figure 4.

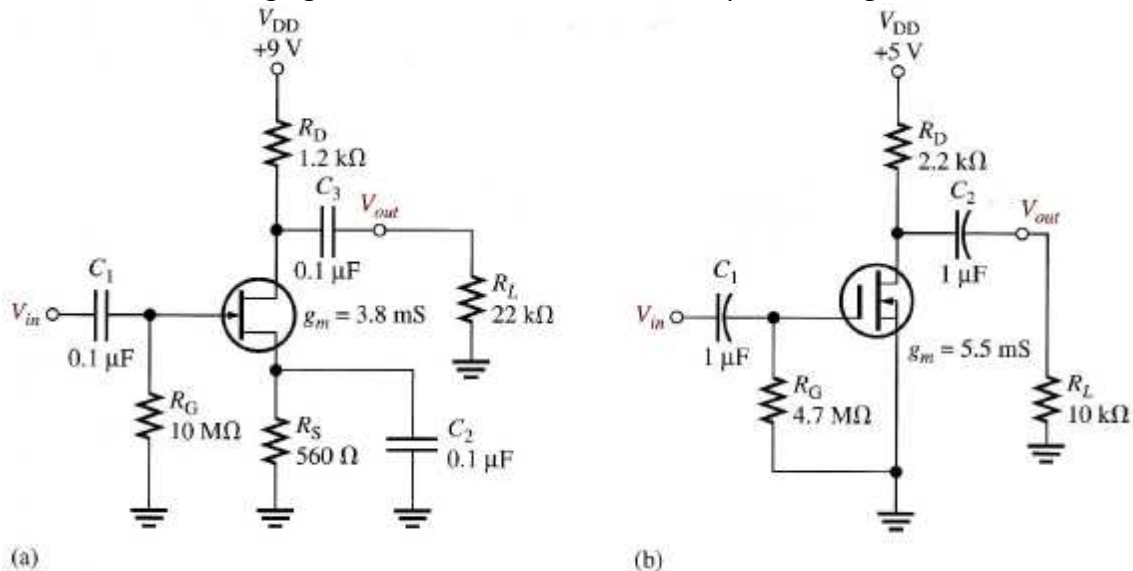


Figure 4

(a) $A_v = g_m R_d = g_m (R_D \parallel R_L) = 3.8\ \text{mS} (1.2\ \text{k}\Omega \parallel 22\ \text{k}\Omega) = 3.8\ \text{mS} (1138\ \Omega) = 4.32$

(b) $A_v = g_m R_d = g_m (R_D \parallel R_L) = 5.5\ \text{mS} (2.2\ \text{k}\Omega \parallel 10\ \text{k}\Omega) = 5.5\ \text{mS} (1.8\ \text{k}\Omega) = 9.92$

11. For the common-source amplifier in Figure 5:

- (a) Calculate I_D , V_{GS} , and V_{DS} for a centered Q-point. $I_{DSS} = 9 \text{ mA}$ and $V_{GS(off)} = -3\text{V}$.
- (b) If a 10 mV rms signal is applied to the input of the amplifier, calculate the rms value of the output signal.

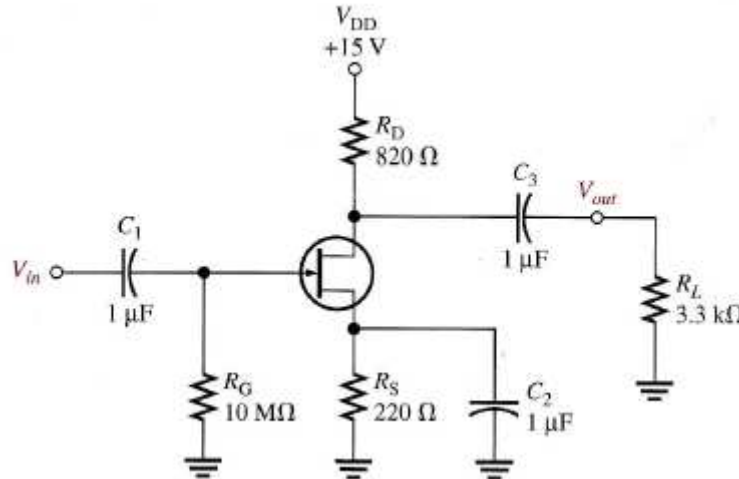


Figure 5

(a)

$$I_D = \frac{I_{DSS}}{2} = \frac{9 \text{ mA}}{2} = 4.5 \text{ mA}$$

$$V_{GS} = -I_D R_S = -(4.5 \text{ mA})(330 \Omega) = -1.49 \text{ V}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S) = 9 \text{ V} - (4.5 \text{ mA})(1.33 \text{ k}\Omega) = 3 \text{ V}$$

(b)

$$A_v = g_m R_d = g_m (R_D \parallel R_L) = 3700 \mu\text{S}(1.0 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = 3700 \mu\text{S}(909 \Omega) = 3.36$$

$$V_{out} = A_v V_{in} = (3.36)(10 \text{ mV}) = 33.6 \text{ mV rms}$$

12. For the unloaded amplifier in Figure 6, calculate I_D , V_{GS} , and V_{DS} , and the rms output voltage V_{ds} . Given = 8 mA at $V_{GS} = 12 \text{ V}$, $V_{GS(th)} = 4\text{V}$ and $g_m = 4500 \mu\text{S}$.

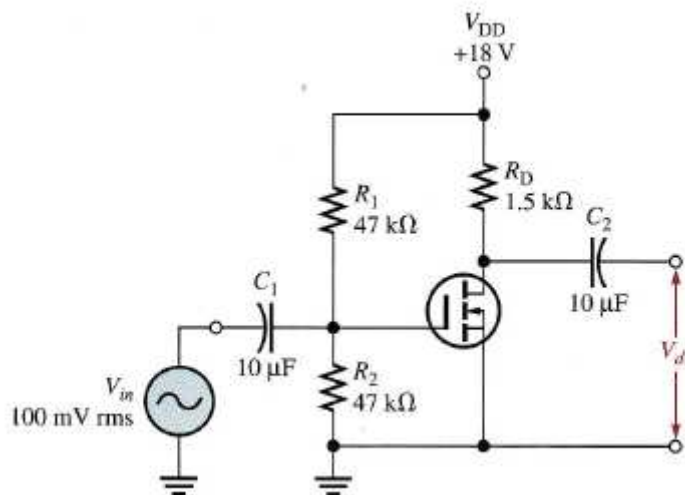


Figure 6

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{47 \text{ k}\Omega}{94 \text{ k}\Omega} \right) 18 \text{ V} = 9 \text{ V}$$

$$K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{8 \text{ mA}}{(12 \text{ V} - 4 \text{ V})^2} = 0.125 \text{ mA/V}^2$$

$$I_{D(on)} = K(V_{GS} - V_{GS(th)})^2 = 0.125 \text{ mA/V}^2 (9 \text{ V} - 4 \text{ V})^2 = 3.13 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_D = 18 \text{ V} - (3.125 \text{ mA})(1.5 \text{ k}\Omega) = 13.3 \text{ V}$$

$$A_v = g_m R_D = 4500 \mu\text{S}(1.5 \text{ k}\Omega) = 6.75$$

$$V_{ds} = A_v V_{in} = 6.75(100 \text{ mV}) = 675 \text{ mV rms}$$

13. For the source-follower (common-drain amplifier) in Figure 7, calculate the voltage gain and input resistance. $I_{GSS} = 50 \text{ pA}$ at $V_{GS} = -15 \text{ V}$ and $g_m = 5500 \mu\text{S}$.

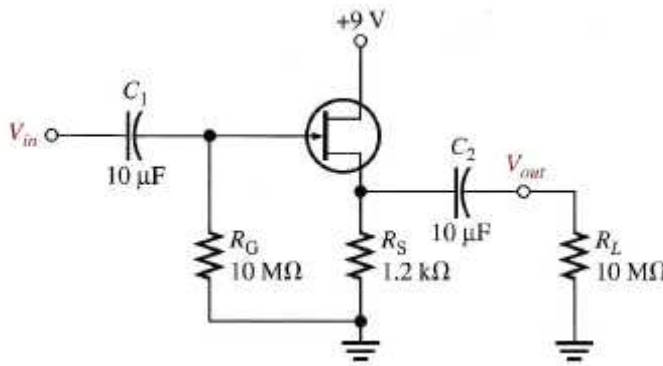


Figure 7

$$R_s = 1.2 \text{ k}\Omega \parallel 10 \text{ M}\Omega \cong 1.2 \text{ k}\Omega$$

$$A_v = \frac{g_m R_s}{1 + g_m R_s} = \frac{(5500 \mu\text{S})(1.2 \text{ k}\Omega)}{1 + (5500 \mu\text{S})(1.2 \text{ k}\Omega)} = 0.868$$

$$R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \left| \frac{-15 \text{ V}}{50 \text{ pA}} \right| = 3 \times 10^{11} \Omega$$

$$R_{in} = 10 \text{ M}\Omega \parallel 3 \times 10^{11} \Omega \cong 10 \text{ M}\Omega$$

14. Calculate the gain if a common-gate amplifier has a $g_m = 4000 \mu\text{S}$ and $R_d = 1.5 \text{ k}\Omega$.

$$A_v = g_m R_d = 4000 \mu\text{S}(1.5 \text{ k}\Omega) = 6.0$$

15. Consider the common-gate amplifier circuit in Figure 8:

- Calculate voltage gain and input resistance of the amplifier.
- For the unloaded amplifier in Figure 8, calculate its voltage gain and input resistance

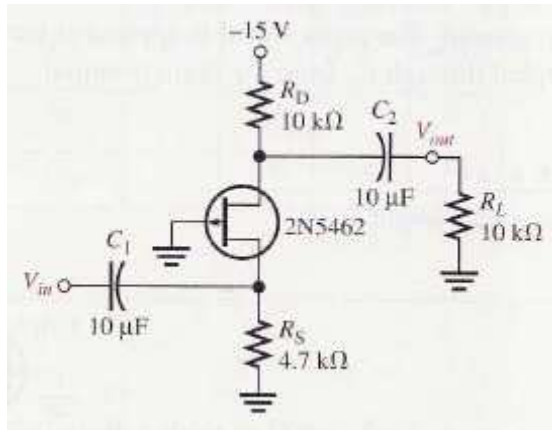


Figure 8

(a) Voltage gain and input resistance of the amplifier:

From data sheet 2N5460 p-channel JFET, $g_m = 2000 \mu\text{S}$ minimum.

This common-gate amplifier has a load resistor, so the effective drain resistance is $R_D \parallel R_L$ and the minimum voltage gain, A_v :

$$A_v = g_m(R_D \parallel R_L) \\ = (2000 \mu\text{S})(10 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = \mathbf{10}$$

The input resistance at the source terminal is

$$R_{in(\text{source})} = 1/g_m = 1/2000 \mu\text{S} = 500 \Omega$$

The signal source actually sees R_S in parallel with $R_{in(\text{source})}$, so the total input resistance is

$$R_{in} = R_{in(\text{source})} \parallel R_S \\ = 500 \Omega \parallel 4.7 \text{ k}\Omega = \mathbf{452 \Omega}$$

(b) For the unloaded amplifier

$$A_v = g_m R_D \\ = (2000 \mu\text{S})(10 \text{ k}\Omega) = \mathbf{20}$$

$$R_{in} = R_{in(\text{source})} \parallel R_S \\ = 500 \Omega \parallel 4.7 \text{ k}\Omega = \mathbf{452 \Omega}$$